

## LAB#3

( Due: See course web page )

Instructor: Dr. Choon Kim


### Objective

- Based on the experience from LAB#1&2, learn how to design, simulate, synthesize, program on FPGA and test **FSM(Finite State Machine)** digital system using Altera Quartus II CAD SW and DE1 FPGA board.
- Learn and become familiar with logic design using **Verilog Hardware Description Language**

### Instructions

1. Your LAB#3 project name should be **L3Cyyy**, where yyy=your CID(e.g., **L3C079** if your CID=079). The golden solution .pof and .sof files are provided. **Student should play with golden solution as a reference whenever he/she has a question during design.**

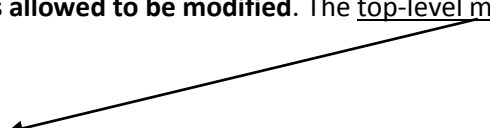2. Use Verilog HDL design. Use the following Verilog top-level module interface code for your design. **No part of this code is allowed to be modified.** The top-level module name must be same as your LAB project name.



```
module L3Cyyy(           // where yyy=your CID. For example, L3C079 if your CID=079
    input  [9:0] sw,      // ten up-down switches, SW9 - SW0
    input  [3:0] key,     // four pushbutton switches, KEY3 - KEY0
    input   clock,       // 24MHz clock source on Altera DE1 board
    output [9:0] ledr,    // ten Red LEDs, LEDR9 - LEDR0
    output [7:0] ledg,    // eight Green LEDs, LEDG8 - LEDG0
    output reg [6:0] hex0, hex1, hex2, hex3    // four 7-segment, HEX3 - HEX0
);
```

3. Like LAB#2, our acceptable timing margin for real-time clock operation is -30 and +30%.

# Soda VM(Vending Machine) Controller Design

\*\*\*\*\*



A vending machine company requests you to design a soda Vending Machine(VM) controller circuit following specifications below. The price of a soda was set to **35 cents**.

## LAB#3 Project Operation Flow

**Warning:** Following operations are \*\*\*prerequisite\*\*\* conditions. You will get **zero(0) point** for LAB#3 if you fail these operations.

- 1) **Initial setting before turning on power:** Whenever you turn on power, you must always make the following initial setting before turning on power.
  - all sw are in DOWN position
  - no key is PRESSED
- 2) When the power is turned on, your design is in **initial state** with following conditions:
  - all leds(i.e., ledg and ledr) are OFF
  - VM is disabled
  - HEX[3:0] displays your CID. For example, HEX[3:0]=**0097** if your CID=097  
(Reminder: Golden solution has HEX[3:0]=0353 since it's CID=353)
- 3) To start VM from the **initial state**:  
Press key[3] once. The hex[3:0] should display "**0000**" as an initial display.
- 4) To stop VM and return to **initial state**:  
Turn off power first. Then turn on power(with initial setting).

# VM Operation Specifications

(Reminder: You should check with golden solution for more details or whenever necessary)

## 1) How to deposit money to VM:

Money deposit to VM is made by **setting up amount of money first** followed by **pressing EnterKey**.

Setting up amount of money

```
sw[8]    // 1 for Reset input (=clearing Deposit balance to 0)
sw[4]    // 1 for Credit-card input(= makes 35 cents immediately regardless of current balance)
sw[3]    // 1 for One-dollar bill input
sw[2]    // 1 for Quarter input
sw[1]    // 1 for Dime input
sw[0]    // 1 for Nickel input
```

Enter key

```
key[3]    // one pressing deposits above money input amount one time.
```

## 2) HEX[3:0] Display Specifications:

**IF** sw[9] = 0 {

**IF** special cases (See 4. Special cases) {

        hex[3:1] = "**Err** "

        hex[0] = off

    }

**ELSE** { // normal operation...

        hex[3:2] = Deposit balance. It displays value up to "**35**"(when dispensing occurs ).

        hex[1:0] = Change balance e.g., **15**

        e.g., hex[3:0]=**3515** when 50 cents were deposited

    }

}

**ELSE IF** sw[9] = 1 (with all other sw are down) {

- hex[0] displays the total number of dispensing made only by **coin input** since board power was turned on.
- The number must be in hexadecimal using modulo-16 format.
- DO NOT make One-dollar-bill input or Credit-card input before testing **sw[9]=1** function. This is a test for only coin input condition!
- hex[3:1] = all OFF
- This operation should **NOT CHANGE** the value of other variables in your design, such as Deposit balance or Change balance.

}

## 3) ledr[9:0] --- dispensing indicator

- All blinking(**half-second period** with **50% duty cycle**) when dispensing,
- All OFF when NOT dispensing

#### 4) Special cases: Your design should be able to handle the following special cases

4.1) \*\*\*\*Multiple inputs case: \*\*\*\*

When more than one sw are UP among sw[0,1,2,3,4,8] AND EnterKey is pressed, hex[3:0] should display "**Err**". For example, sw[2]=sw[3]= 1.

4.2) \*\*\*\*Consecutive one-dollar bill inputs or Consecutive credit-card inputs case: \*\*\*\*

Two consecutive one-dollar bill inputs or Two consecutive credit-card inputs should display "**Err**" on hex[3:0]. For example, one-dollar bill input followed by one-dollar bill input, or credit-card input followed by credit-card input.

(However, note that one-dollar bill input followed by credit-card input, or credit-card input followed by one-dollar bill input is O.K.)

4.3) \*\*\*\*Credit Card input when hex[3:0]=3500(i.e., when Deposit=35 and Change=00) \*\*\*\*

This is another case when hex[3:0] should display "**Err**".

The "**Err**" display is cleared to "0000"(=Deposit and Change balance are and cleared to zero) by either pressing EnterKey or Reset input. Then normal operation can continue.

## Checking Items during Demo

**Warning:** **ledr[9:0] blinking operation**(See Sec.3) is a dispensing indicator. Therefore it must be working correctly during demo. You will get **zero(0)** point for the **Part** if the ledr[9:0] blinking operation does not work correctly.

**PART 1**(3 pts) : **Coin input** operation

**PART 2**(3 pts) : **sw[9] = 1** (with all other sw are down) operation

**PART 3**(3 pts) : **Credit-card** and **Reset** operations

**PART 4**(3 pts) : **One-dollar bill** operation

**PART 5**(3 pts) : **"Err"** display operation